

SOLUTION FOR MORE EXERCISES FOR MIDTERM # 2

1. (Flip-Flops)

a. What is the difference between a latch and a flip flop?

SOLUTION:

Latch is a level sensitive device.

Flip-flops are edge sensitive devices.

b. Implement a JK flip-flop with a T flip-flop and a minimal AND-OR-NOT network.

Let us assume that the complements of J, K and Q signals are available. Draw the logic diagram to show your design.

SOLUTION:

Step 1: write the next state table

JK flip-flop next state table

J	K	Q _{current}	Q _{next}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

T flip-flop excitation table

T	Q _{current}	Q _{next}
0	0	0
0	1	1
1	0	1
1	1	0


Step 2: derive the excitation table from the next state tables

Excitation table

J	K	Q _{current}	T
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1


Step 3: derive next state logic

$$T = JQ' + KQ$$

 

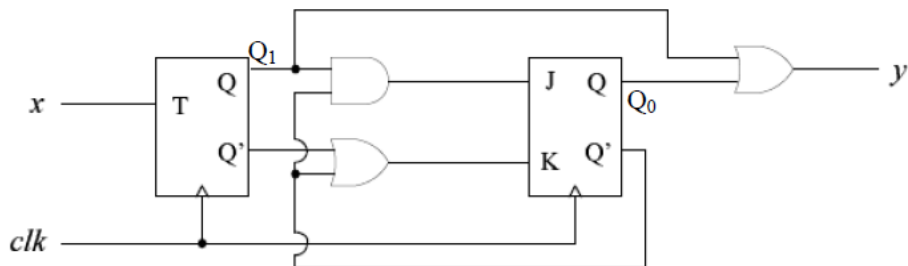2. (Design Specification)

Write the state table of the sequential circuit as the following figure.



SOLUTION:

From the circuit we directly get

$$T = x$$

$$J = Q_1Q_0'$$

$$K = Q_1' + Q_0'$$

$$y = Q_1 + Q_0$$

We use these equations to get $Q_1(t+1)$ and $Q_0(t+1)$:

$Q_1 Q_0$	T	$Q_1(t+1)$	J	K	$Q_0(t+1)$
00	0	0	0	1	0
01	1	1	0	1	0
10	0	0	1	1	1
11	1	0	1	1	1
00	0	0	0	1	0
01	1	1	0	1	0
10	0	1	1	1	1
11	1	0	0	0	1
11	1	0	0	0	1

Finally, the State table:

Q ₁ Q ₀	Next state		Output (y)	
	X=0	X=1	X=0	X=1
00	00	10	0	0
01	00	10	1	1
10	11	01	1	1
11	11	01	1	1

3. (Sequential Circuit Design)

A state machine is described by the following state equations:

$$Q_1(t+1) = Q_0(t) \oplus x(t),$$

$$Q_0(t+1) = Q_1(t)x'(t) + Q_0(t)x(t),$$

$$y(t) = Q_1'(t) + Q_0(t).$$

a. Write the state table

SOLUTION:

2-bit states: Q₁, Q₀

1 input: x

1 output: y

X	Q ₁ (t)	Q ₀ (t)	Q ₁ (t+1)	Q ₀ (t+1)	y
0	0	0	0	0	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	1	1	1
1	0	0	1	0	1
1	0	1	0	1	1
1	1	0	1	0	0
1	1	1	0	1	1

b. Design the system with two JK flip-flops and a minimal AND-OR-NOT network.

X	Q ₁ (t)	Q ₀ (t)	Q ₁ (t+1)	Q ₀ (t+1)	J ₁	K ₁	J ₀	K ₀	y
0	0	0	0	0	0	X	0	X	1
0	0	1	1	0	1	X	x	1	1
0	1	0	0	1	x	1	1	X	0
0	1	1	1	1	x	0	x	0	1
1	0	0	1	0	1	X	0	X	1
1	0	1	0	1	0	X	x	0	1
1	1	0	1	0	x	0	0	X	0
1	1	1	0	1	x	1	x	0	1

Kmap for J1

		Q1Q0			
		00	01	11	10
X	0	0	1	x	x
	1	1	0	x	x

$$J_1 = X'Q_0 + XQ_0'$$

Kmap for K1

		Q1Q0			
		00	01	11	10
X	0	x	x	0	1
	1	x	x	1	0

$$K_1 = X'Q_0' + XQ_0$$

Kmap for J0

		Q1Q0			
		00	01	11	10
X	0	0	x	x	1
	1	0	x	x	0

$$J_0 = X'Q_1$$

Kmap for K0

		Q1Q0			
		00	01	11	10
X	0	x	1	0	x
	1	x	0	0	x

$$K_0 = X'Q_1'$$

Kmap for y

		Q1Q0			
		00	01	11	10
X	0	1	1	1	0
	1	1	1	1	0

$$y = Q_1' + Q_0$$

4. (Timing)

In the following circuit

Each flip flop has:

Setup time of 60ps

Hold time of 20ps


Clock-to-Q maximum delay of 70ps

Clock-to-Q minimum delay of 50ps

Each XOR gate has:

Propagation delay of 100ps

Contamination delay of 55ps

 

- a. If there is no clock skew, what is the maximum operating frequency of this circuit?

SOLUTION:

$$T_c \geq T_{pcq} + T_{pd} + T_{setup}$$

Longest path:

$$T_c \geq T_{pcq} + 3 \cdot T_{pd} + T_{setup}$$

$$T_c \geq 70 + 3 \cdot 100 + 60 = 430 \text{ ps}$$

$$\text{Max Frequency} = 1/T_c = 2.33 \text{ GHz}$$

- b. How much clock skew can the circuit tolerate before it might experience a hold time violation?

SOLUTION:

$$T_{ccq} + T_{cd} \geq T_{hold} + T_{skew}$$

Shortest Path:

$$T_{ccq} + T_{cd} \geq T_{hold} + T_{skew}$$

$$50 + 55 \geq 20 + T_{skew}$$

$$T_{skew} \leq 85 \text{ ps}$$

- c. Redesign the circuit so that it can be operated at 3GHz frequency. How much clock skew can your circuit tolerate before it might experience a hold time violation?


SOLUTION:

$$T_c \geq T_{pcq} + 2 \cdot T_{pd} + T_{setup} + T_{skew}$$

$$T_c \geq 330 + T_{skew}$$

$$T_{ccq} + 2T_{cd} \geq T_{hold} + T_{skew}$$

$$T_{skew} \leq 140 \text{ ps}$$

 


5. (Decoders and Multiplexers)

Given a three-input Boolean function $f(a; b; c) = \sum m(0, 1, 2, 3, 7)$.

a. Implement the function using a minimal network of 2:4 decoders and OR gates.

SOLUTION:


$$f = a' + bc$$

 

b. Implement the function using a minimal network of 4:1 multiplexers.

SOLUTION:

$$F = a'b' + a'b + abc$$

 

c. Implement the function using a minimal network of 2:1 multiplexers.

SOLUTION:

